

Started on Wednesday, 3 July 2024, 5:30 AM

State Finished

Completed on Wednesday, 3 July 2024, 5:36 AM

Time taken 6 mins 10 secs

Grade 6.00 out of 10.00 (60%)

Question 1

Incorrect

Mark 0.00 out of 1.00

How many outputs does a 2-to-4 decoder have?

- ☒ a. 2 ✖
- ☐ b. 3
- ☐ c. 4
- ☐ d. 8

Question 2

Correct

Mark 1.00 out of 1.00

To implement a 2-input AND gate, you need:

- ☒ a. Two NAND gates ✔
- ☐ b. Two NOR gates
- ☐ c. Two XOR gates
- ☐ d. Two OR gates

Your answer is correct.

Question 3

Incorrect

Mark 0.00 out of 1.00

A 4-to-1 multiplexer has:

- ☒ a. 2 control inputs ✖
- ☐ b. 3 control inputs
- ☐ c. 4 control inputs
- ☐ d. 5 control inputs

Your answer is incorrect.

Question 4

Correct

Mark 1.00 out of 1.00

How many outputs does a 3-to-8 decoder have?

- ☐ a. 2
- ☐ b. 3
- ☒ c. 8 ✓
- ☐ d. 6

Question 5

Incorrect

Mark 0.00 out of 1.00

A 4-variable Karnaugh map has how many cells in total?

- ☒ a. 4 ✗
- ☐ b. 8
- ☐ c. 16
- ☐ d. 32

Question 6

Correct

Mark 1.00 out of 1.00

The output of a 4-input OR gate is 0 only when:

- ☒ a. All inputs are 0 ✓
- ☐ b. All inputs are 1
- ☐ c. Any of the inputs is 1
- ☐ d. All inputs are X (undefined)

Question 7

Correct

Mark 1.00 out of 1.00

In a combinational circuit:

- ☒ a. The output depends on the current input only ✓
- ☐ b. The output depends on the current and previous inputs
- ☐ c. The output depends on the current and future inputs
- ☐ d. The output depends on the internal state of the circuit

Your answer is correct.

Question 8

Incorrect

Mark 0.00 out of 1.00

A decoder is a combinational circuit that ____.

- ☐ a. Converts a binary number to a decimal numberX (undefined)
- ☒ b. Converts a decimal number to a binary number | ✖
- ☐ c. Converts a binary number to a set of outputs
- ☐ d. Converts a set of outputs to a binary number

Question 9

Correct

Mark 1.00 out of 1.00

In a 3-to-8 decoder, how many input lines are there?

- ☒ a. 3 ✓
- ☐ b. 8
- ☐ c. 11
- ☐ d. 5

Your answer is correct.

Question 10

Correct

Mark 1.00 out of 1.00

What is the maximum number of select lines required for a 16-to-1 multiplexer?

- ☐ a. 3
- ☒ b. 4 ✓
- ☐ c. 8
- ☐ d. 16