

inputs. The half adder can be implemented using basic gates such as [XOR](#) and [AND](#) gates.



Sure, here's a more in-depth explanation of the half adder circuit:

The half adder is a basic building block for more complex adder circuits such as full adders and multiple-bit adders. It performs binary addition of two single-bit inputs, A and B, and provides two outputs, SUM and CARRY.

The SUM output is the least significant bit (LSB) of the result, which is the [XOR](#) of the two inputs A and B. The [XOR gate](#) implements the addition operation for [binary digits](#), where a "1" is generated in the SUM output only when one of the inputs is "1".



Adobe Creative Cloud



Half Adder (HA):

Half adder is the simplest of all adder circuits. Half adder is a combinational arithmetic circuit that adds two numbers and produces a sum bit (s) and

Aptitude Engineering Mathematics Discrete Mathematics Operating System DBMS Computer Networks

carry bit (c). Both the output variables are sum & carry bits. A and B are the two input bits.

let us consider two input bits A and B, then sum bit (s) is the X-OR of A and B. it is evident from the function of a half adder that it requires one X-OR gate and one AND gate for its construction.

Truth Table:

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Here we perform two operations Sum and Carry, thus we need two K-maps



Sum = A XOR B

For Carry:

		A	
		0	1
B	0	0	0
	1	0	1

Carry = A AND B

Implementation:



2.Speed: The half viper works at an extremely rapid, making it reasonable for use in fast computerized circuits.

Disadvantages of Half Adder in Digital Logic :

1.Limited Usefulness: The half viper can add two single-piece numbers and produce a total and a convey bit. It can't perform expansion of multi-bit numbers, which requires the utilization of additional intricate circuits like full adders.

2.Lack of Convey Info: The half snake doesn't have a convey input, which restricts its value in more mind boggling expansion tasks. A convey input is important to perform expansion of multi-bit numbers and to chain numerous adders together.

3.Propagation Deferral: The half snake circuit has a proliferation delay, which is the time it takes for the result to change in light of an adjustment of the info. This can cause timing issues in computerized circuits, particularly in fast frameworks.

Application of Half Adder in Digital Logic:

1.Arithmetic circuits: Half adders are utilized in number-crunching circuits to add double numbers. At the point when different half adders are

"GeeksforGeeks helped me ace the GATE exam! Whenever I had any doubt regarding any topic, GFG always helped me and made my concepts quiet clear." - [Anshika Modi](#) | AIR 21



Choose GeeksforGeeks as your perfect [GATE](#) 2025 Preparation partner with these newly launched programs

[GATE CS & IT- Online](#)

[GATE DS & AI- Online](#)

[GATE Offline \(\[Delhi\]\(#\)/NCR\)](#)

Over 150,000+ students already trust us to be their [GATE](#) Exam guide. Join them & let us help you in opening the GATE to top-tech IITs & NITs!



GeeksforGeeks

138

Previous Article

Two Level Implementation of Logic Gates

Next Article

Full Adder in Digital Logic

Similar Reads

Difference between Half Adder and Full Adder

In this article, we will go through the Difference between the Half adder and

4 min read



BCD Adder in Digital Logic

BCD stands for binary coded decimal. It is used to perform the addition of BCD numbers. A BCD digit can have any of ten possible four-bit representations....

2 min read

[View More Articles](#)

Article Tags :

[Digital Logic](#)





Languages

Python
Java
C++
PHP
GoLang
SQL
R Language
Android Tutorial
Tutorials Archive

Data Science & ML

Data Science With Python
Data Science For Beginner
Machine Learning Tutorial
ML Maths
Data Visualisation Tutorial
Pandas Tutorial
NumPy Tutorial
NLP Tutorial
Deep Learning Tutorial

Python Tutorial

Python Programming Examples
Python Projects
Python Tkinter
Web Scraping
OpenCV Tutorial

DSA

Data Structures
Algorithms
DSA for Beginners
Basic DSA Problems
DSA Roadmap
Top 100 DSA Interview Problems
DSA Roadmap by Sandeep Jain
All Cheat Sheets

HTML & CSS

HTML
CSS
Web Templates
CSS Frameworks
Bootstrap
Tailwind CSS
SASS
LESS
Web Design

Computer Science

Operating Systems
Computer Network
Database Management System
Software Engineering
Digital Logic Design

Preparation Corner

Company-Wise Recruitment Process
Resume Templates
Aptitude Preparation
Puzzles
Company-Wise Preparation

Management & Finance

Management
HR Management
Finance
Organisational Behaviour
Marketing

More Tutorials

Software Development
Software Testing
Product Management
SEO - Search Engine Optimization
Linux
Excel
All Cheatsheets

School Subjects

Mathematics
Physics
Chemistry
Biology
Social Science
English Grammar
World GK

Free Online Tools

Typing Test
Image Editor
Code Formatters
Code Converters
Currency Converter
Random Number Generator
Random Password Generator

GeeksforGeeks Videos

DSA
Python
Java
C++
Web Development
Data Science
CS Subjects

@GeeksforGeeks, Sanchhaya Education Private Limited, All rights reserved

