

Started on Monday, 8 July 2024, 7:40 AM

State Finished

Completed on Monday, 8 July 2024, 7:46 AM

Time taken 5 mins 20 secs

Grade 7.00 out of 10.00 (70%)

Question 1

Correct

Mark 1.00 out of 1.00

A JK flip-flop can be used to implement:

- ☒ a. Counters ✓
- ☐ b. Multiplexers
- ☐ c. Decoders
- ☐ d. Adders

Question 2

Correct

Mark 1.00 out of 1.00

The clock signal in flip-flops is used for:

- ☐ a. Data transmission
- ☐ b. Resetting the flip-flop
- ☒ c. Synchronizing operations ✓
- ☐ d. Powering the flip-flop

Question 3

Incorrect

Mark 0.00 out of 1.00

Which type of flip-flop is used in shift registers?

- ☐ a. SR flip-flop
- ☐ b. D flip-flop
- ☐ c. T flip-flop
- ☒ d. JK flip-flop ✗

Question 4

Incorrect

Mark 0.00 out of 1.00

Sequential circuits are distinguished from combinational circuits by the presence of:

- ☐ a. Clock signals
- ☐ b. Memory elements
- ☐ c. Logic gates
- ☒ d. Multiplexers ✖

Your answer is incorrect.

Question 5

Correct

Mark 1.00 out of 1.00

What is a typical use of a register in a computer system?

- ☐ a. Storing the program instructions
- ☒ b. Storing temporary data during arithmetic or logic operations ✔
- ☐ c. Performing data routing in the ALU
- ☐ d. Controlling the clock signal

Your answer is correct.

Question 6

Correct

Mark 1.00 out of 1.00

The output of a T flip-flop with $T=1$ is:

- ☐ a. 0
- ☐ b. 1
- ☒ c. Toggle ✔
- ☐ d. Undefined

Question 7

Correct

Mark 1.00 out of 1.00

The purpose of the clock signal in sequential circuits is to:

- ☐ a. provide power
- ☒ b. synchronize operations ✓
- ☐ c. amplify signals
- ☐ d. provide external input

Question 8

Correct

Mark 1.00 out of 1.00

What is a fundamental difference between a latch and a flip-flop?

- ☒ a. Latches are level-sensitive, while flip-flops are edge-sensitive ✓
- ☐ b. Latches are edge-triggered, while flip-flops are level-triggered
- ☐ c. Latches have clock inputs, while flip-flops do not
- ☐ d. Latches are synchronous, while flip-flops are asynchronous

Your answer is correct.

Question 9

Correct

Mark 1.00 out of 1.00

Which flip-flop has an additional input called the enable input?

- ☒ a. D flip-flop ✓
- ☐ b. SR flip-flop
- ☐ c. JK flip-flop
- ☐ d. T flip-flop

Question 10

Incorrect

Mark 0.00 out of 1.00

Which gate is used to implement the clock signal for flip-flops?

- ☐ a. AND gate
- ☐ b. OR gate
- ☐ c. XOR gate
- ☒ d. NOT gate ✗

